


# Experiment 2 – Frequency Regulator

Mohadeseh  
Azari,  
810196404

**Abstract**— this lab is about changing in frequency, first of all let's see what does that mean, "changing in frequency". Well, in the previous lab we've talked about one of the most important role in digital logic design, and that was the clock. We introduced lots of different ways to build the clock; But the problem is that our clock frequency is not a constant value and there are lots of factors that can affect its frequency. Changing in frequency is a crucial issue because synchronisation between the clocks is as important as the clocks themselves. In [part1](#) we design a frequency regulator to change the initial value and so the frequency and finally in [part2](#) we synthesis our design and change the value of set Period.


**Keywords**— synchronisation, frequency, adjusted clock

## I. DESIGN DESCRIPTION AND SYNTHESIS

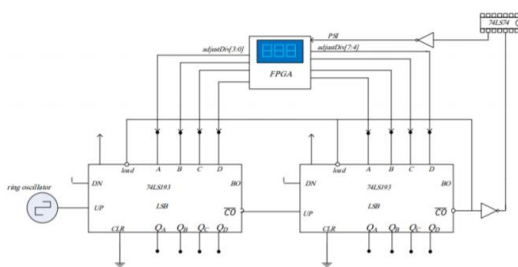

Clock Adjusting System

 The processor should calculate the input frequency and compare it with a desired reference signal. If the reference and the input's frequencies are not the same, then it should change the division value.



Frequency regulator pins

### Decide\_when\_to\_count\_and\_count


```
15 always @(posedge clk, posedge rst) begin: decide_when_to_count_and_count
16   if(rst)
17     duration<=9'b0;
18   else begin
19     case({previous_PSI, PSI})
20       2'b01 : duration<=9'b0;           //zero to one
21       2'b11 : duration<=duration+1;     //steady at one
22       2'b10 : duration<=duration;       //one to zero
23       2'b00 : duration<=duration;       //steady at zero
24     endcase
25   end
26 end
27
```

### Comparison


```
28 always@(negedge PSI) begin: comparison
29   inc<=1'b0;
30   dec<=1'b0;
31   if({previous_PSI, PSI}==2'b10)
32     if(duration>{1'b0, setPeriod})
33       dec<=1'b1;
34   else if(duration<setPeriod)
35     inc<=1'b1;
36 end
37
```
 
### Increment\_decrement

```
38 always@(posedge clk, posedge rst) begin: increment_decrement
39   if(rst)
40     adjustedDiv<=8'b01111111;
41   else begin
42     if({previous_PSI, PSI}==2'b10)
43       if(inc==1'b1) begin
44         adjustedDiv<=adjustedDiv+1;
45       end
46     else if(dec==1'b1) begin
47       adjustedDiv<=adjustedDiv-1;
48     end
49   end
50 end
51 end
52 end
53 end
54 end
55
```




Frequency regulator

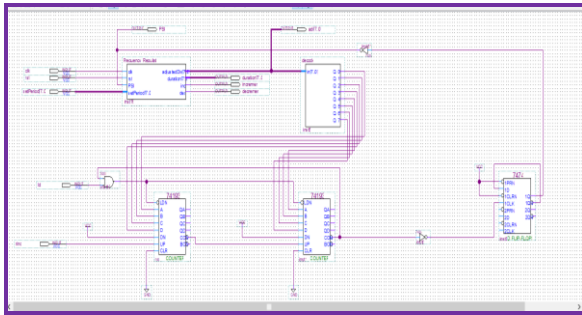

Schematic design

## II. DESIGN SIMULATION IN MODELSIM

 


Test bench for 20MHz clock

/TB/dk	1
/TB/rst	0
/TB/d	1
/TB/set	01111101
/TB/PSI	St0
/TB/ring	1
/TB/adj	11001101
/TB/increment	St1
/TB/decrement	St0
/TB/duration	00111111

Output signals


Zoom in:

 

As we can see the set Period is 01111101(125) and the duration value is 01111111(127) so the duration is higher than the set period and as you can see the increment signal gets one and our initial value that once was 11001100(204) is now 11001101(205).


Ring Oscillator	Desired Frequency	Final Parallel Loads	Initial Parallel Loads	Set period	Invert Delay
20 MHz	400 kHz	205	127	125	8.4
30 MHz	400 kHz	180	127	125	5.6
40 MHz	400 kHz	155	127	122	4.17

Zoom in:

 

the set Period is 01111101(125) and the duration value is 01111100(124) so the duration is lower than the set period and as you can see the decrement signal gets one and our initial value that once was 10110101(181) is now 11001101(180).

Zoom in:

 

the set Period is 01111101(125) and the duration value is 01111110(126) so the duration is higher than the set period and as you can see the increment signal gets one and our initial value that once was 10011000(152) is now 10011010(154).

. Calculation ☹

$$\frac{\text{Ring Oscillator Frequency}}{\text{modulo}} = 400 * 10^3$$

$$255 - \text{modulo} = \text{initial}$$

Frequency		
20 MHz	$\frac{20 * 10^6}{400 * 10^3} = 50$	255-50=205
30MHz	$\frac{30 * 10^6}{400 * 10^3} = 75$	255-75=180
40MHz	$\frac{40 * 10^6}{400 * 10^3} = 100$	255-100 = 155

### III. CONCLUSION

the conclusion after this lab was one easy way to reduce the effects of Asynchronizations between the clocks by simply insert an FPGA module to change the initial value.